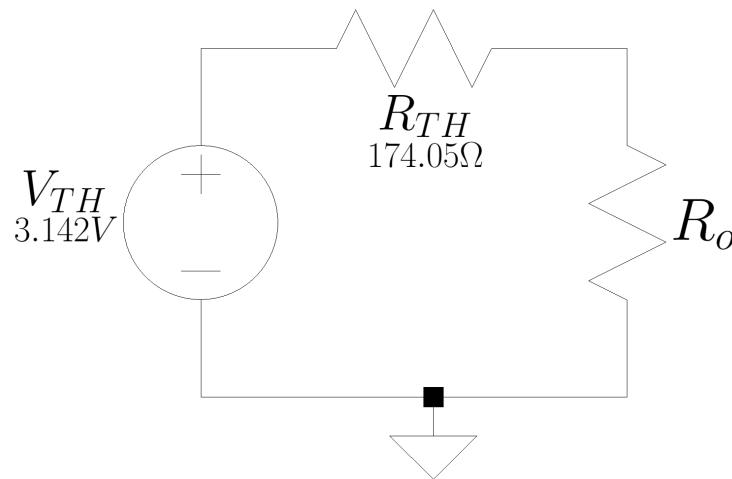



i.

The measured value of the Thevenin voltage,  $V_{TH}$ , is equal the voltage measured across  $V_o$  after creating an open circuit, and is measured to be  $3.142V$ . The Thevenin resistance,  $R_{TH}$ , is calculated from creating a short circuit across the voltage source and then finding the equivalent resistance across the circuit (excluding  $R_o$ ).  $R_{TH} = (R1||R2||R4||R5) = 174.05\Omega$ .



ii.

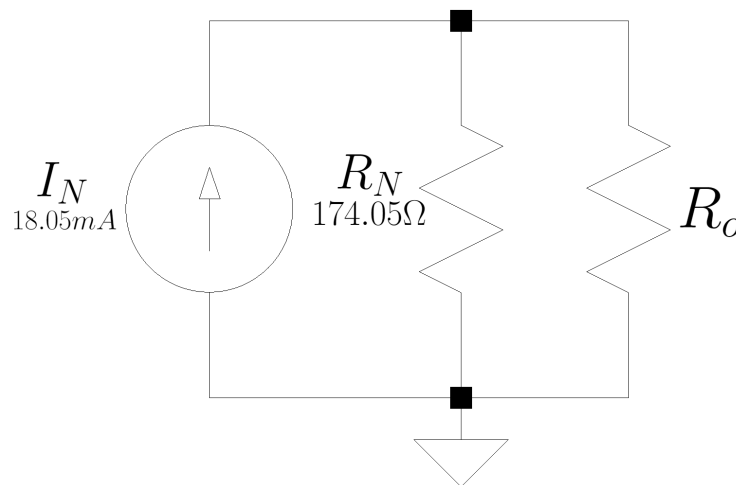The value of  $I_N$  is equal to the value of the  $I_{SC}$  when the Thevenin equivalent circuit is short circuited at the load, therefore  $I_N = I_{SC} = \frac{V_{TH}}{R_{TH}} = \frac{3.142V}{174.05\Omega} = 18.05mA$ . The Norton resistance,  $R_N$ , is equal to the Thevenin resistance of the Thevenin equivalent circuit, therefore  $R_N = R_{TH} = 174.05\Omega$ .



iii.

The value of  $R_o$  that would allow for the maximum power transfer in this circuit is  $174.05\Omega$ . This is because the derivative of the power in a Thevenin/Norton circuit is equal to zero when the load resistance is equal to the Thevenin/Norton resistance.

iv.

$$P_{max} = I^2 R_o = \left( \frac{V}{R_o + R_{TH}} \right)^2 R_o = \left( \frac{3.142}{174.05 + 174.05} \right)^2 174.05 = 14.18mW$$

The maximum power transfer in the circuit is  $14.18mW$ .

v.

The theoretical value for  $R_{TH}$  can be calculated by creating a short circuit around the voltage source and then finding the equivalent resistance of the circuit (excluding the load resistor,  $R_o$ ).  $R_{TH} = (R1 \parallel R2 \parallel R4 \parallel R5) = (220 \parallel 1k \parallel 10k \parallel 10k) = 174.05\Omega$ . The theoretical value for  $V_{TH}$  can be found by creating an open circuit around  $V_o$  and calculating the open circuit voltage. We can use nodal analysis, there is a single node with voltage at that node equal to the open circuit voltage,  $V_{oc}$ .

$$\left[ \frac{1}{220} + \frac{1}{1k} + \frac{1}{10k} + \frac{1}{10k} \right] [V_1] = \left[ \frac{4V}{220} \right]$$

$$[V_1] = \left[ \frac{1}{220} + \frac{1}{1k} + \frac{1}{10k} + \frac{1}{10k} \right]^{-1} \left[ \frac{4V}{220} \right]$$

$$[V_1] = [3.1642V]$$

After performing nodal analysis, we can see that  $V_{TH} = V_1 = 3.1642V$ . The measured value of  $V_{TH}$ ,  $3.142V$ , is very similar to the calculated value of  $V_{TH}$ ,  $3.1642V$ .

vi.

The resistor used had a resistance of  $220\Omega$ . The voltage for the Thevenin circuit using a similar resistance to the Thevenin resistance is similar to the voltage of the original circuit.

