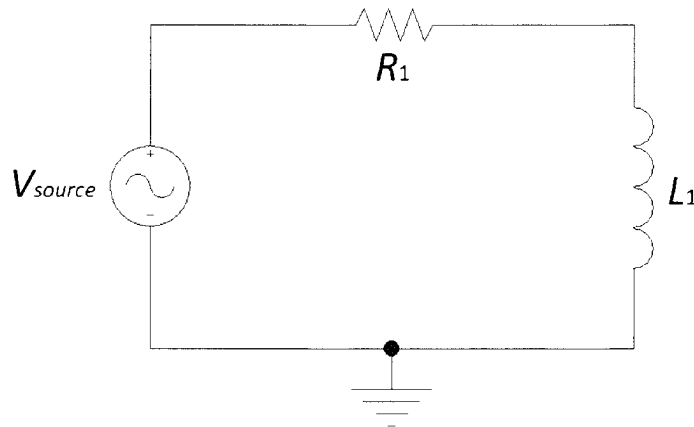


Experiment:

- i. Given the following circuit, with $R_1 = 100\Omega$, $L_1 = 1\text{mH}$, and an input waveform $V_{source} = \cos(\omega t)$, with a frequency of 100kHz , calculate the current through the inductor with respect to time.



- ii. Build the circuit from part i in Capture CIS Lite, and excite the circuit with a sinusoidal waveform with a frequency $\text{FREQ} = 100\text{kHz}$, an amplitude $\text{VAMPL} = 1\text{V}$, $\text{VOFF} = 0$, and $\text{AC} = 0$. Set the simulation time to $200\mu\text{s}$ and add a trace for the inductor voltage and the current through the inductor. Set the x-axis to user defined, $80\mu\text{s}$ to $110\mu\text{s}$. (This allows the inductor current to reach steady state conditions). Include a screenshot in your report.
- iii. What is the amplitude of the inductor current based on your simulation results?
- iv. Build the circuit from part i on a breadboard, with the same attributes for R_1 , L_1 , and the source voltage. Using the oscilloscope tool, plot the inductor voltage on channel 1, and the inductor current using a math channel. Include a screenshot in your report.
- v. Using a vertical measurement in the oscilloscope tool, measure the phase difference between the inductor voltage and the inductor current.
- vi. How do the three waveforms (calculated, simulated, actual) compare with one another?
- vii. What occurs in a series RLC circuit when the input is set to the resonance frequency?