


$$I_T = \frac{V_{Th}}{R_{Th} + R_o} = \frac{3.416 V}{1.926 k\Omega + 1 k\Omega} = 1.167 mA$$

Then the power dissipated in R_o can be calculated as follows:

$$P = I_T^2 R_o = (1.167 mA)^2 \cdot 1 k\Omega = 1.362 mW$$

Experiment:

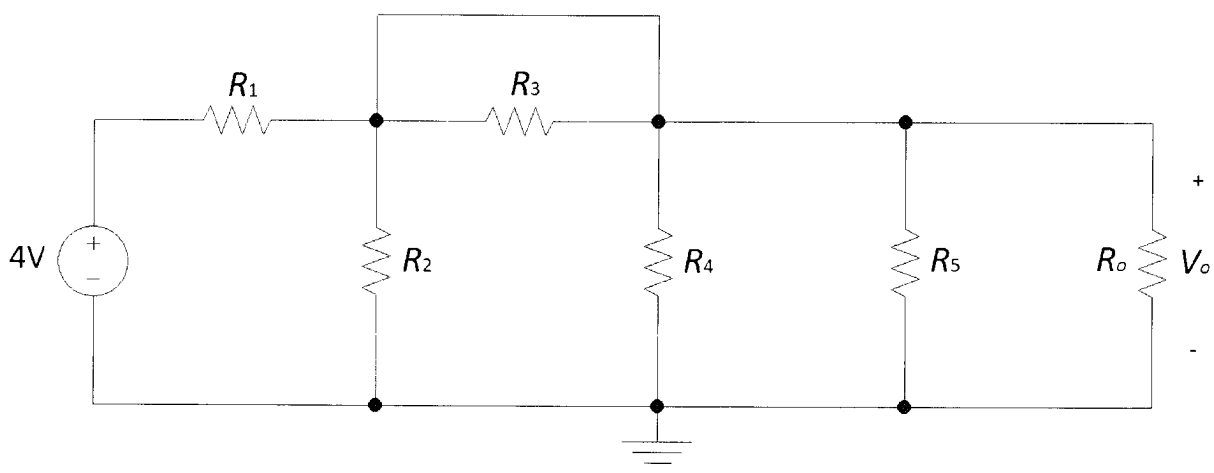- i. Given the following circuit, and that $R_1 = 220\Omega$, $R_2 = R_5 = 10k\Omega$, $R_3 = 100k\Omega$, $R_4 = 1k\Omega$, build the circuit and measure the required values to generate the Thevenin equivalent circuit at R_o . Draw the Thevenin equivalent circuit using your measured values and include it in your report.
Note: Do not disassemble the circuit, it will be used again in part vi.



- ii. Using the same circuit from part i, generate the Norton equivalent circuit at R_o . Draw the Norton equivalent circuit using your measured values and include it in your report.
- iii. What value of R_o would allow for maximum power transfer in this circuit, and why?

- iv. Calculate the maximum power transfer in the circuit using the value determined in part iii.
- v. Compute the theoretical values for the Thevenin equivalence of the circuit from part i to confirm the measured values from part i.
- vi. Given $R_o = 1\text{k}\Omega$, plot V_o for the original circuit from part I on channel 1 of the oscilloscope on the Analog Discovery 2. Proceed to build the Thevenin equivalent circuit using the closest resistor to R_{Th} . Plot V_o on channel 2 of the oscilloscope using the same R_o and compare to V_o measured from the original circuit. Include a screenshot of the oscilloscope showing channel 1 and 2 in your report.