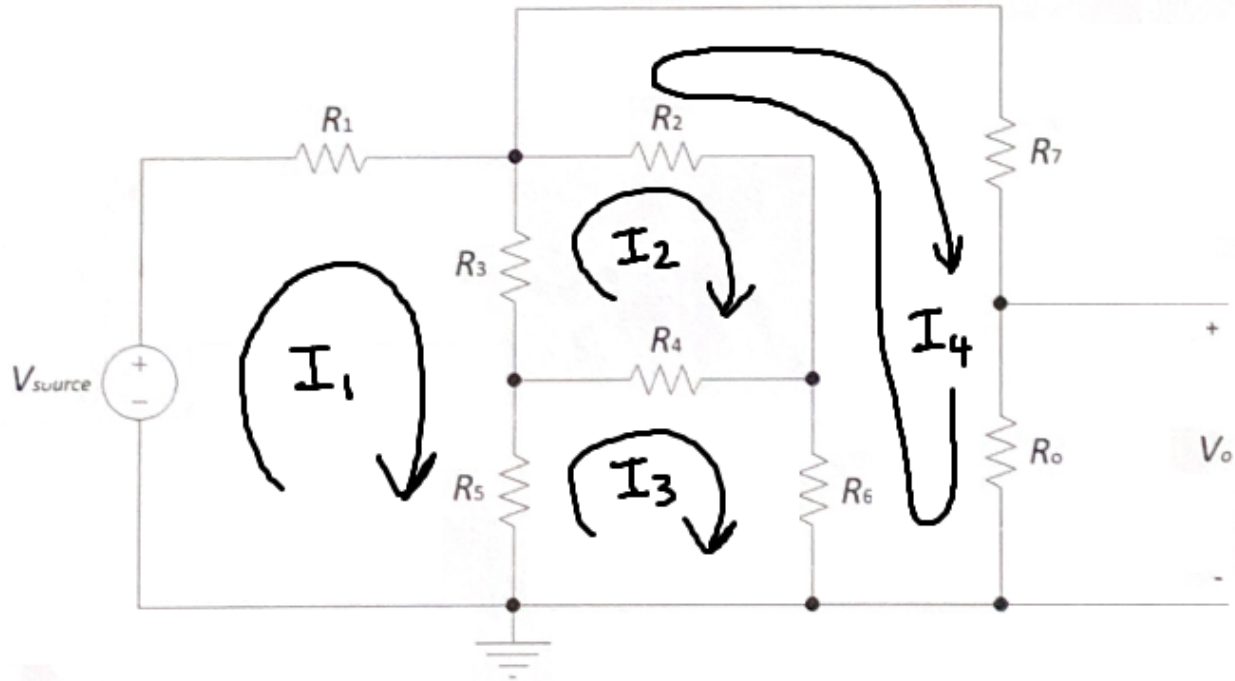


i.



Loop 1

$$\begin{aligned} R_1 I_1 + R_3(I_1 - I_2) + R_5(I_1 - I_3) &= V_{source} \\ (R_1 + R_3 + R_5)I_1 - R_3 I_2 - R_5 I_3 + 0I_4 &= V_{source} \end{aligned} \quad (1)$$

Loop 2

$$\begin{aligned} R_2(I_2 - I_4) + R_3(I_2 - I_1) + R_4(I_2 - I_3) &= 0 \\ -R_3 I_1 + (R_2 + R_3 + R_4)I_2 - R_4 I_3 - R_2 I_4 &= 0 \end{aligned} \quad (2)$$

Loop 3

$$\begin{aligned} R_4(I_3 - I_2) + R_5(I_3 - I_1) + R_6(I_3 - I_4) &= 0 \\ -R_5 I_1 - R_4 I_2 + (R_4 + R_5 + R_6)I_3 - R_6 I_4 &= 0 \end{aligned} \quad (3)$$

Loop 4

$$\begin{aligned} R_2(I_4 - I_2) + R_6(I_4 - I_3) + R_7 I_4 + R_o I_4 &= 0 \\ 0I_1 - R_2 I_2 - R_6 I_3 + (R_2 + R_6 + R_7 + R_o)I_4 &= 0 \end{aligned} \quad (4)$$

$$\begin{matrix} (1) \\ (2) \\ (3) \\ (4) \end{matrix} \begin{bmatrix} (R_1 + R_3 + R_5) & -R_3 & -R_5 & 0 \\ -R_3 & (R_2 + R_3 + R_4) & -R_4 & -R_2 \\ -R_5 & -R_4 & (R_4 + R_5 + R_6) & -R_6 \\ 0 & -R_2 & -R_6 & (R_2 + R_6 + R_7 + R_o) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} V_{source} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} (R_1 + R_3 + R_5) & -R_3 & -R_5 & 0 \\ -R_3 & (R_2 + R_3 + R_4) & -R_4 & -R_2 \\ -R_5 & -R_4 & (R_4 + R_5 + R_6) & -R_6 \\ 0 & -R_2 & -R_6 & (R_2 + R_6 + R_7 + R_o) \end{bmatrix}^{-1} \begin{bmatrix} V_{source} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

ii.

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} (R_1 + R_3 + R_5) & -R_3 & -R_5 & 0 \\ -R_3 & (R_2 + R_3 + R_4) & -R_4 & -R_2 \\ -R_5 & -R_4 & (R_4 + R_5 + R_6) & -R_6 \\ 0 & -R_2 & -R_6 & (R_2 + R_6 + R_7 + R_o) \end{bmatrix}^{-1} \begin{bmatrix} V_{source} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} =$$

$$\begin{bmatrix} (220\Omega + 1k\Omega + 1k\Omega) & -1k\Omega & -1k\Omega & 0 \\ -1k\Omega & (1k\Omega + 1k\Omega + 10k\Omega) & -10k\Omega & -1k\Omega \\ -1k\Omega & -10k\Omega & (10k\Omega + 1k\Omega + 10k\Omega) & -10k\Omega \\ 0 & -1k\Omega & -10k\Omega & (1k\Omega + 10k\Omega + 10k\Omega + 24.7k\Omega) \end{bmatrix}^{-1} \begin{bmatrix} 4V \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 2.227\text{mA} \\ 0.535\text{mA} \\ 0.409\text{mA} \\ 0.101\text{mA} \end{bmatrix}$$

iii.

	$I_{calculated}$ (mA)	$I_{measured}$ (mA)
I_1	2.227	2.22
I_2	0.535	0.550
I_3	0.409	0.420
I_4	0.101	0.0995

iv.

$$V_o = I_4 R_o = 0.101\text{mA} \times 24.7k\Omega = 2.495V$$

The calculated value of V_o is 2.495V. The measured value of V_o is 2.482V.

v.

$$P_o = \frac{V_o^2}{R_o}$$

$$P_{o_{calculated}} = \frac{V_{o_{calculated}}^2}{R_o} = \frac{2.495^2}{24.7k} = 0.252mW$$

$$P_{o_{measured}} = \frac{V_{o_{measured}}^2}{R_o} = \frac{2.482^2}{24.7k} = 0.249mW$$

The calculated value of P_o using the calculated value of V_o is 0.252mW. The calculated value of P_o using the measured value of V_o is 0.249mW.

vi.

The measured value of V_o is 0.310V. The calculated value of P_o is 0.0961mW.

$$P_{o_{measured}} = \frac{V_o^2}{R_o} = \frac{0.310^2}{1k} = 0.0961mW$$

vii.

